

18.2.2021

BILKENT UNIVERSITY
COMPUTER ENGINEERING DEPT.
CS223 LAB 2 SECTION 4

LAB REPORT




ZÜBEYİR BODUR
21702382

Spring 2021


1. Circuit Schematics

For all IC's, their pin number for GND is 7 and for Vcc(+5V) is 14. Proper pin numbers are drawn on top of each port.


a) 1 bit Full Adder

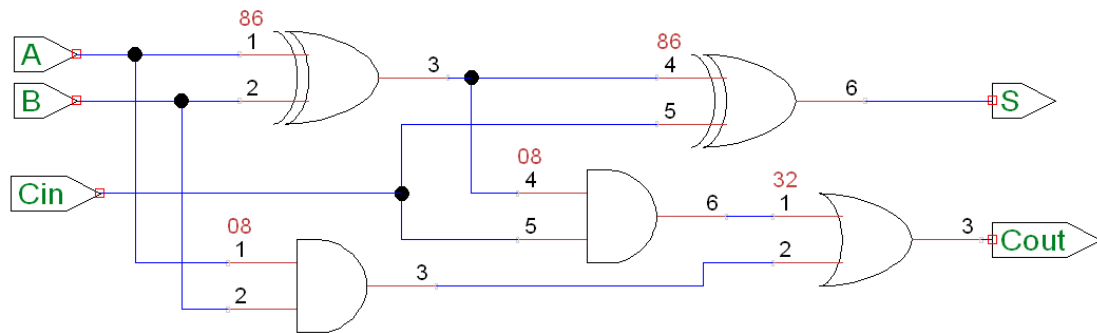

b) 2 bit Full Adder

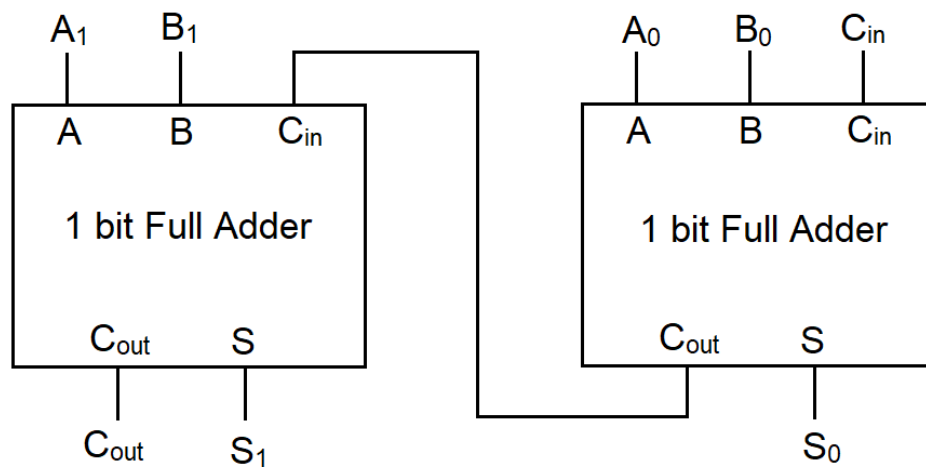

 This design can be represented in a single black box:



2. SystemVerilog Modules & Testbenches

a) Dataflow - 1 bit Full Adder

```
module adder1D(input logic a, b, c_in,
               output logic s, c_out
);
    assign s = a ^ b ^ c_in;
    assign c_out = a & b | a & c_in | b & c_in;
endmodule
```

```
module testadder1D();
    logic c_in, c_out;
    logic a, b, s;
    integer i, j, k;
    adder1D uut(.a(a),
                .b(b),
                .c_in(c_in),
                .s(s),
                .c_out(c_out)
    );
    initial begin
        a <= 0;
        b <= 0;
        c_in <= 0;
        for(i = 0; i < 2; i = i + 1) begin
            for (j = 0; j < 2; j = j + 1) begin
                for (k = 0; k < 2; k = k + 1) begin
                    #10 c_in <= c_in + 1;
                end
                b <= b + 1;
            end
            a <= a + 1;
        end
    end
endmodule
```

b) Structural - 1 bit Full Adder

```
module adder1S( input logic a, b, c_in,
                output logic s, c_out
                );
    logic a_xor_b, a_and_b, c_in_and_axorb;
    xor2 xor_1(a_xor_b, a, b);
    xor2 xor_2(s, a_xor_b, c_in);
    and2 and_1(a_and_b, a, b);
    and2 and_2(c_in_and_axorb, c_in, a_xor_b);
    or2 or_(c_out, a_and_b, c_in_and_axorb);
endmodule
```

```
module testadder1S();
    logic c_in, c_out;
    logic a, b, s;
    integer i, j, k;
    adder1S uut( .a(a),
                 .b(b),
                 .c_in(c_in),
                 .s(s),
                 .c_out(c_out)
                 );
    initial begin
        a <= 0;
        b <= 0;
        c_in <= 0;
        for(i = 0; i < 2; i = i + 1) begin
            for (j = 0; j < 2; j = j + 1) begin
                for (k = 0; k < 2; k = k + 1) begin
                    #10 c_in <= c_in + 1;
                end
                b <= b + 1;
            end
            a <= a + 1;
        end
    end
endmodule
```

c) Structural - 2 bit Full Adder

```
module adder2S(    input logic[1:0] a, b,
                  input logic c_in,
                  output logic[1:0] s,
                  output logic c_out
);
    logic c_in_1;
    adder1D    zerothbit(a[0],    b[0],    c_in,    s[0],
c_in_1);
    adder1D    firstbit(a[1],    b[1],    c_in_1,    s[1],
c_out);
endmodule
```

```
module testadder2S();
    logic c_in, c_out;
    logic[1:0] a, b, s;
    integer i, j;

    adder2S uut( .a(a),
                  .b(b),
                  .c_in(c_in),
                  .s(s),
                  .c_out(c_out)
);

    initial begin
        a <= 0;
        b <= 0;
        c_in <= 0;
        for(i = 0; i < 4; i = i + 1) begin
            for (j = 0; j < 4; j = j + 1) begin
                #10 b <= b + 1;
            end
            a <= a + 1;
        end
    end
endmodule
```