

04.03.2020

CS 223-4

DIGITAL DESIGN

LAB 2

PRELIMINARY REPORT




ZÜBEYİR BODUR


21702382

Spring 2020


## 1. 1-Bit Full Adder

 

## 2. 1-Bit Full Subtractor

 

## 3. 2-Bit Full Adder

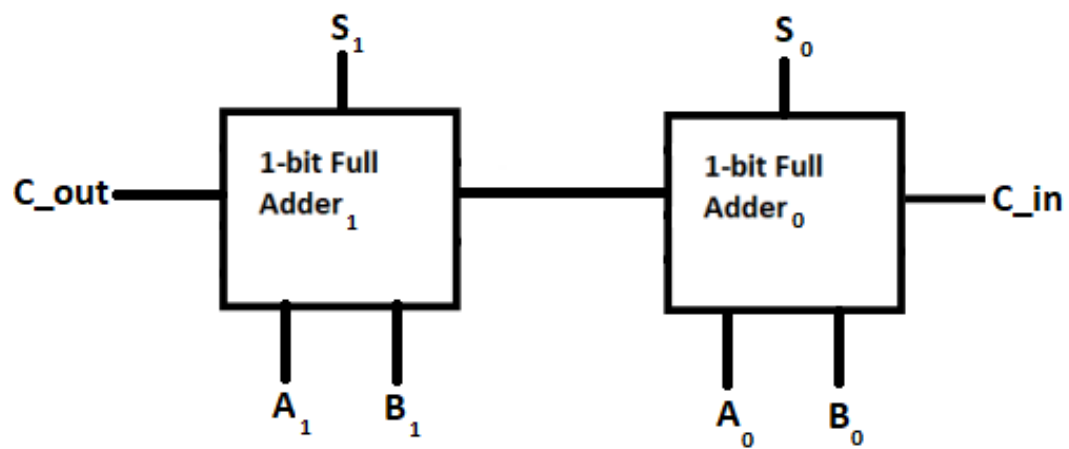

## 4. System Verilog Modules

```
// Behavioral module for one bit full adder
//
module oneBitFullAdder( input logic a, b, c_in,
                      output logic c_out, sum
);
    assign sum = ~a & ~b & c_in | ~a & b & ~c_in
                | a & ~b & ~c_in
                | a & b & c_in;
    assign c_out = b & c_in | a & b | a & c_in;
endmodule
```

```
// Behavioral module for one bit full subtractor
//
module oneBitFullSubtractor( input logic a, b, b_in,
                             output logic b_out, dif
);
    assign dif = ~a & ~b & b_in | ~a & b & ~b_in
                | a & ~b & ~b_in
                | a & b & b_in;
    assign b_out = b & b_in | ~a & b | ~a & b_in;
endmodule
```

```
// Structural module for one bit full adder
//
module fullAdder( input logic a, b, c_in,
                  output logic c_out, sum
);
    oneBitFullAdder adder(a, b, c_in, c_out, sum);
endmodule
```

```
// Structural module for one bit full subtractor
//
module fullSubs( input logic a, b, b_in,
                 output logic b_out, dif
);
    oneBitFullSubtractor subs(a, b, b_in, b_out, dif);
endmodule
```

```
// Structural module for two bit full subtractor
//
module TwoBitAdder( input logic a_1, a_0, b_1, b_0, c_in,
                    output logic c_out, sum_1, sum_0
);
    logic c_out_1;
    fullAdder adder1( a_0, b_0, c_in, c_out_1, sum_0);
    fullAdder adder2( a_1, b_1, c_out_1, c_out, sum_1);
endmodule
```

## 5. Testbenches

```
module testAdder();
    logic a, b, c_in, c_out, sum;
    oneBitFullAdder test( a, b, c_in, c_out, sum);
    initial begin
        a = 0; b = 0; c_in = 0; #10;
        repeat(2) begin
            repeat(2) begin
                repeat(2) begin
                    c_in = ~c_in; #10;
                end
                b = ~b; #10;
            end
            a = ~a; #10;
        end
        $stop;
    end
endmodule
```

```
module testFullAdder();
    logic a, b, c_in, c_out, sum;
    fullAdder test( a, b, c_in, c_out, sum);
    initial begin
        a = 0; b = 0; c_in = 0; #10;
        repeat(2) begin
            repeat(2) begin
                repeat(2) begin
                    c_in = ~c_in; #10;
                end
                b = ~b; #10;
            end
            a = ~a; #10;
        end
        $stop;
    end
endmodule
```

```

module testFullSubtractor();
  logic a, b, b_in, dif, b_out;
  fullSubs test( a, b, b_in, b_out, dif);
  initial begin
    a = 0; b = 0; b_in = 0; #10;
    repeat(2) begin
      repeat(2) begin
        repeat(2) begin
          b_in = ~b_in; #10;
        end
        b = ~b; #10;
      end
      a = ~a; #10;
    end
    $stop;
  end
endmodule

```

```

module testTwoBitAdder();
  logic a_1, a_0, b_1, b_0, c_in, c_out, sum_1, sum_0;
  TwoBitAdder test( a_1, a_0, b_1, b_0, c_in, c_out, sum_1, sum_0 );
  initial begin
    a_1 = 0; a_0 = 0 ; b_1 = 0; b_0 = 0; c_in = 0; #10;
    repeat(2) begin
      repeat(2) begin
        repeat(2) begin
          repeat(2) begin
            b_0 = ~b_0; #10;
          end
          b_1 = ~b_1; #10;
        end
        a_0 = ~a_0; #10;
      end
      a_1 = ~a_1; #10;
    end
    c_in = ~c_in; #10;
  end
  $stop;
end
endmodule

```