

CS-223-02

Lab 1

Zübeyir Bodur

21702382


PRELIMINARY REPORT

4 IC's are used;

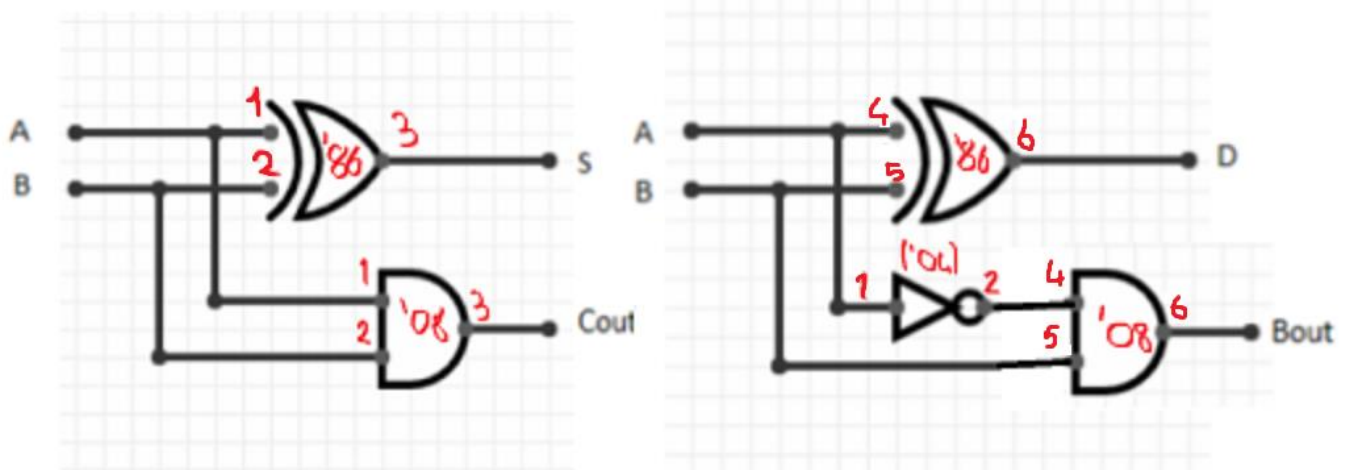1. One 7404 HEXInverting Gate
2. One 7408 Quad-2 Input AND Gate
3. One 7432 Quad-2 Input OR Gate
4. One 7486 Quad-2 Input XOR Gate

and for all IC's, their pin number for GND is 7 and for $V_{cc}(+5V)$ is 14.

Below, there are the circuit schematics for half-adder and half-subtractor in figure 2.




CS-223-02

Lab 1

Zübeyir Bodur

21702382

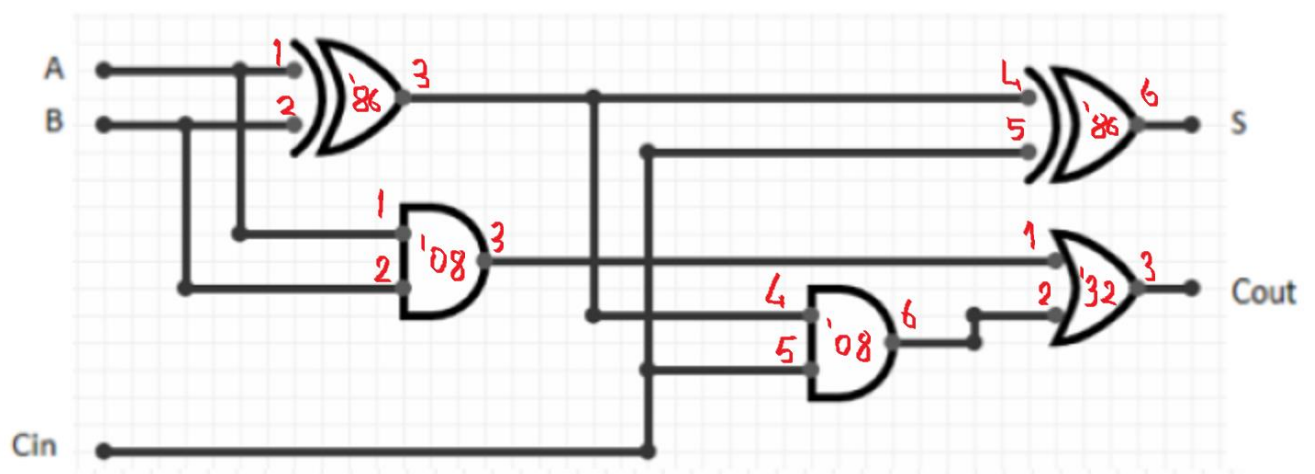Circuit schematics for full-adder (which was in figure 3) is also below.



Finally, this is circuit schematics for the full-subtractor in figure 3.

